 


09 Finite State Machine (FSM) I

- What is a Finite State Machine (FSM)?
- States and their representations
- State Transition Diagram (STD)
- Number of Flip-Flops in System
- Separating Combinational Logic into 2
- State Encoding
- Put it all together into schematics
- Put it all together into Verilog

What is a Finite State Machine (FSM)?



Finite	= less than infinity
Machine	= circuit or system

State	= set of (dynamic) information that is sufficient for the system to work
-------	--

What is a State?

State = set of (dynamic) information that is sufficient for the system to work

Example:

- playing tic-tac-toe:

[\[WIKI\]](#)

		X

O		X

O		X
X		

O		X
	O	
X		

O		X
	O	
X		X

O		X
	O	O
X		X

O		X
	O	O
X	X	X

Each board position is a state:


1. knows result (in progress, X wins, O wins, draw)
2. knows who goes next, X or O
3. can deduce the optimal next move

What is a State?

State = set of (dynamic) information that is sufficient for the system to work

Example:


- playing tic-tac-toe:

 

[WIKI]

FSM example:

Example: - 0, 1, 2, 3 counter

 


c: 0, 1, 2, 3, 0, 1, 2, 3, ...

- every clock cycle, c changes in sequence
- Can this box have M (flip-flops) only? NO
- Can this box have CL only? NO

Box has both CL and M → It is an FSM.

FSM example:

 


c: 0, 1, 2, 3, 0, 1, 2, 3, ...

State	= set of (dynamic) information that is sufficient for the system to work
-------	--

What should the states be?

- current value of c → how many values? 4
- need to store current values of c
→ how many flip flops? 2

FSM example:

 

c: 0, 1, 2, 3, 0, 1, 2, 3, ...

State = set of (dynamic) information that is sufficient for the system to work

- need to store states from one clock cycle to next


State = output of the flip-flops inside circuit

FSM example:


State = set of (dynamic) information that is sufficient for the system to work

State = output of the flip-flops inside circuit


 
Next State = input of the flip-flops inside circuit



FSM example:

 


c: 0, 1, 2, 3, 0, 1, 2, 3, ...

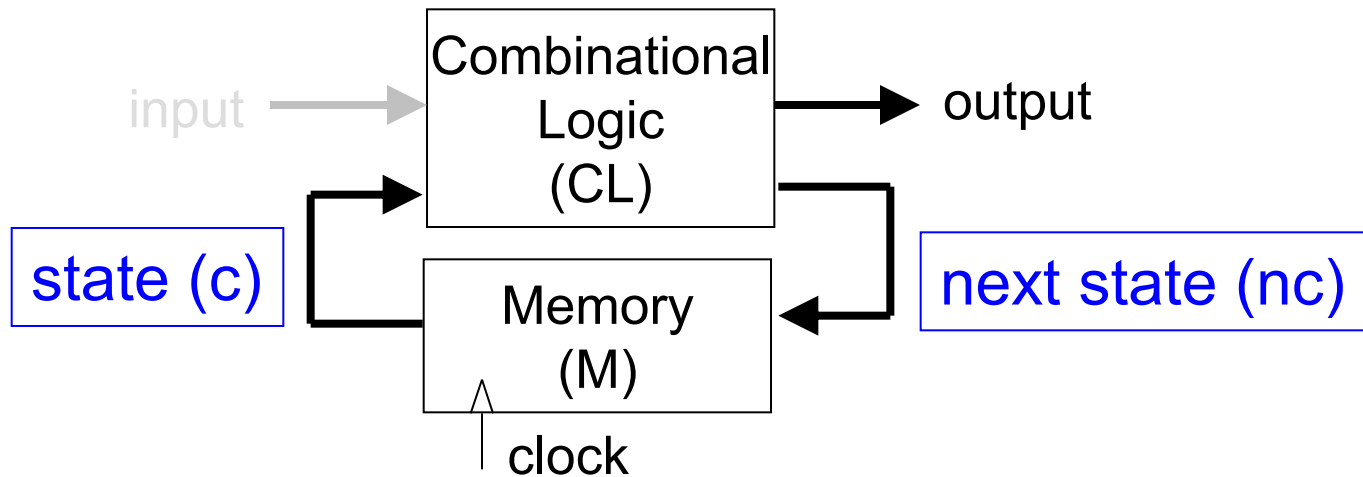 


FSM example: $c: 0, 1, 2, 3, 0, 1, 2, 3, \dots$

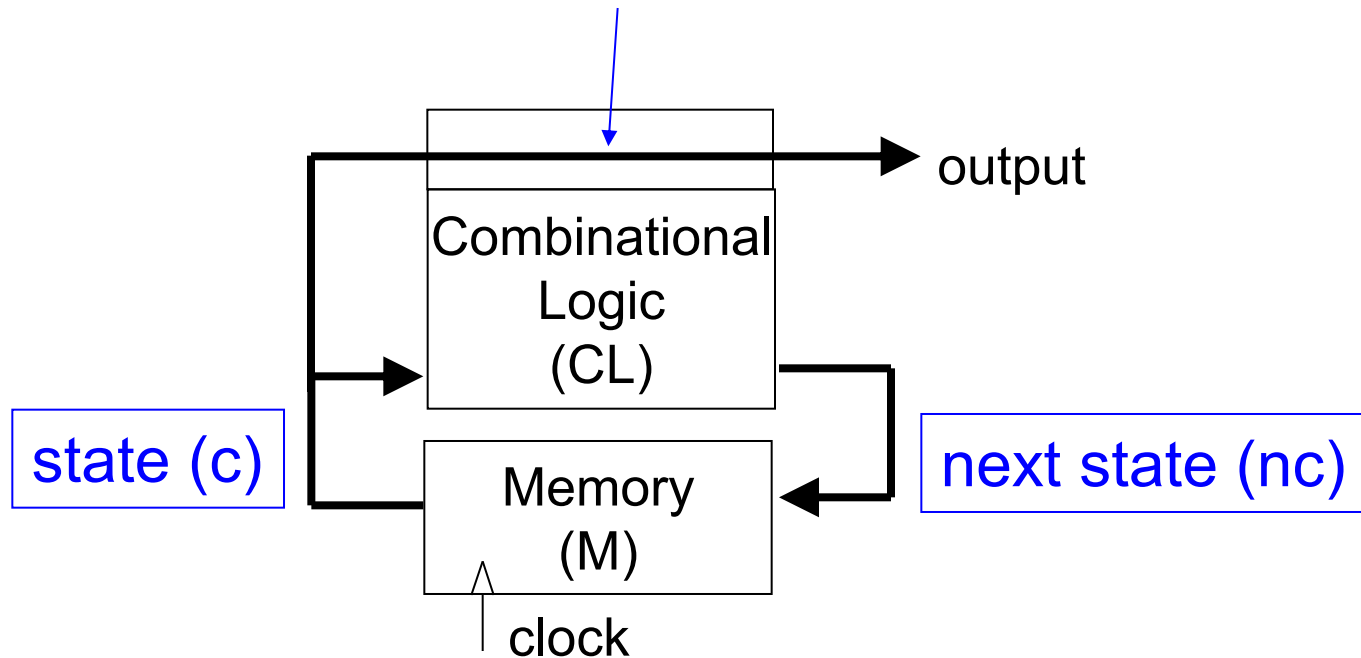a straight wire is also a combinational logic



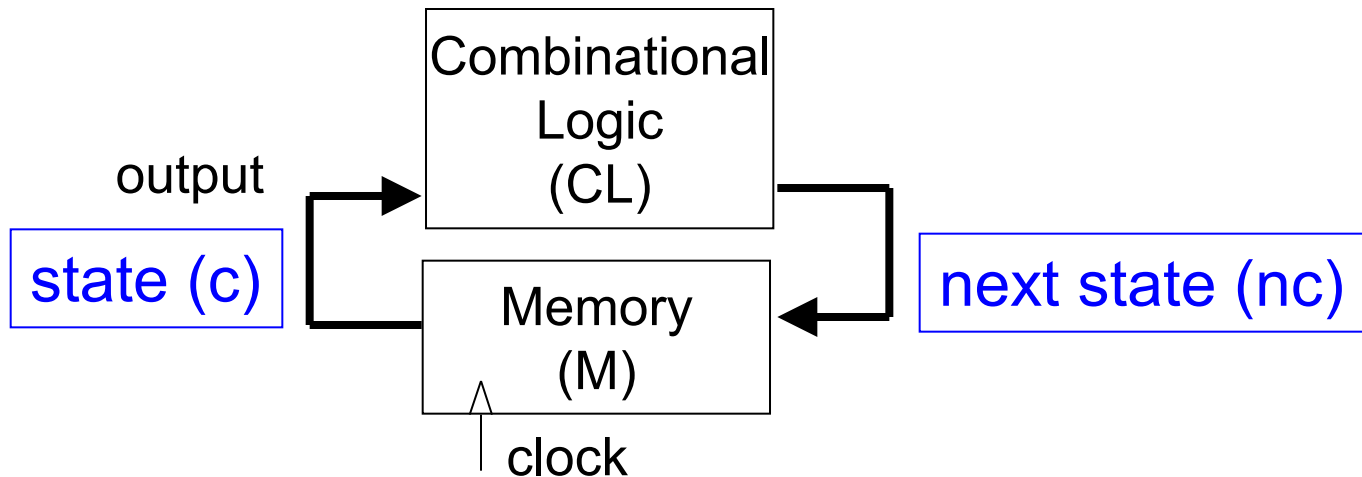FSM example: $c: 0, 1, 2, 3, 0, 1, 2, 3, \dots$




2 persons working in this factory

- CL (Claire): can calculate, but not remember
- M (Mike): can remember, cannot think

one clock period = one day

CLaire works 6am-6pm, Mike 6pm-6am

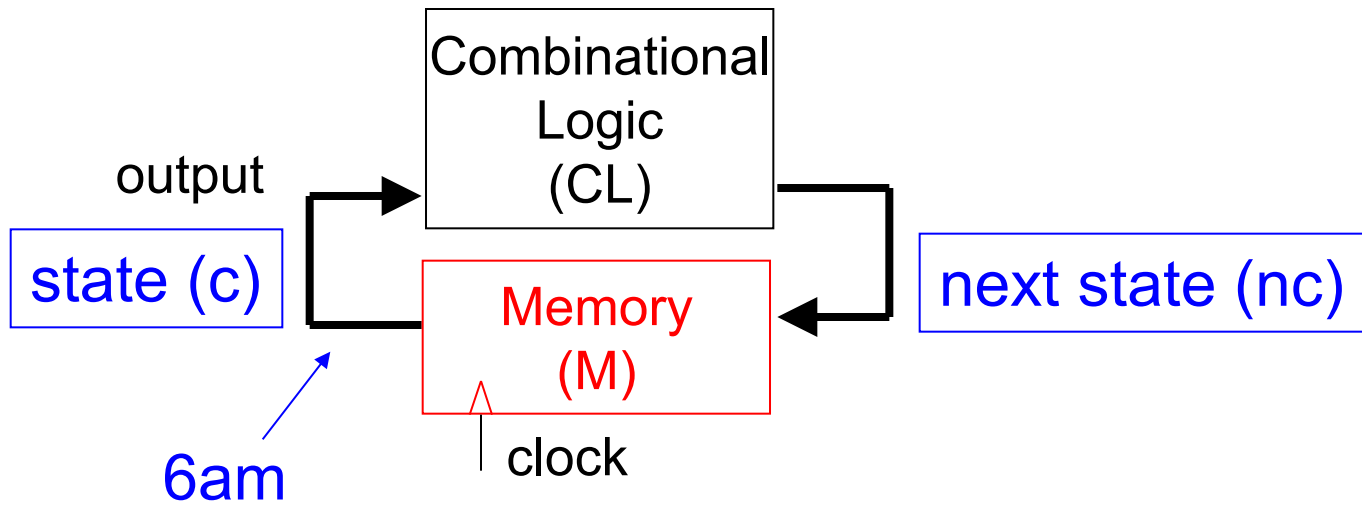
FSM example: $c: 0, 1, 2, 3, 0, 1, 2, 3, \dots$



at 6am

- Mike gives what he remembers from last night to CLaire
(next c from yesterday becomes c today)
- This c is also shown as system output

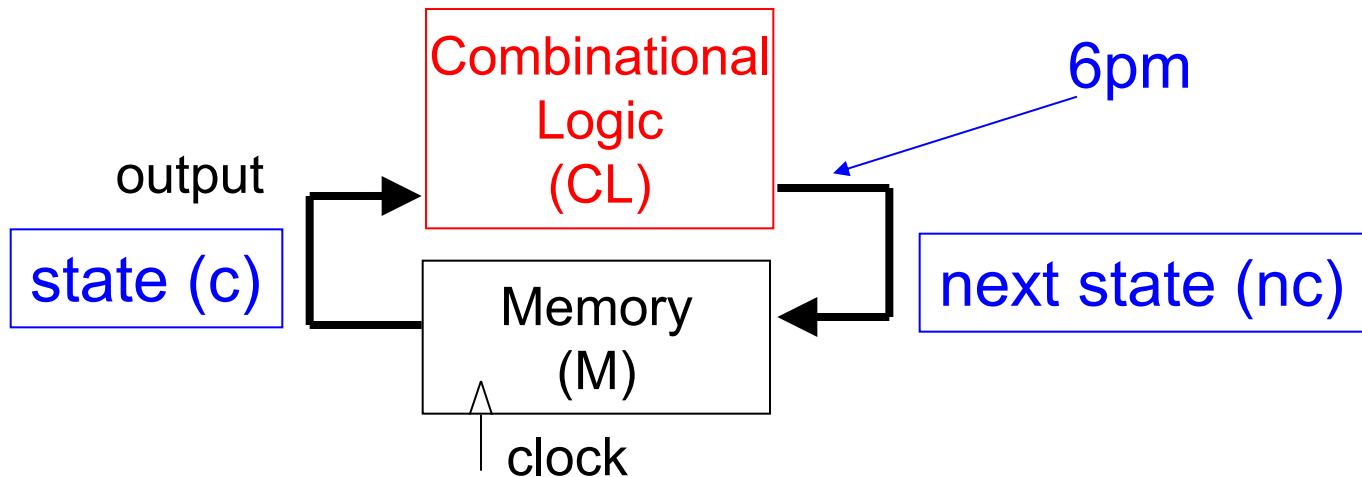
FSM example: $c: 0, 1, 2, 3, 0, 1, 2, 3, \dots$



From 6am-6pm

- CLaire sees c from Mike
- CLaire calculates what next c should be
- at 6pm, CLaire gives **next c** to Mike
- **CLaire does not need to remember next c**

 FSM example: $c: 0, 1, 2, 3, 0, 1, 2, 3, \dots$




What does CLaire do?

- Look at c
 if c is 3, let nc be 0
 else nc is $c+1$

What does Mike do?

- store nc that CLaire gives at 6pm, and give it back to CLaire next morning, calling it c

 FSM example: $c: 0, 1, 2, 3, 0, 1, 2, 3, \dots$




Outsides look at c and see $0, 1, 2, 3, 0, 1, 2, 3, \dots$

Real life circuits:

- Mike takes a very short time to transfer nc to c
- Most of the time, CLaire is working to calculate nc from c

Representing FSM: State Transition Diagram

 State = set of (dynamic) information that is
sufficient for the system to work
= output of the flip-flops inside circuit



c: 0, 1, 2, 3, 0, 1, 2, 3, ...


This system has

- 4 states (0, 1, 2, 3) (requires 2 flops)

State Transition Diagram

- graphical diagram
- shows relationships between current state (s) and next state (ns)
- does NOT represent circuits

SYMBOLS USED:

 


circles = states
one circle per state
write name inside



arcs = arrows = transitions
comes out from current state
and points to next state


State Transition Diagram

 


$c: 0, 1, 2, 3, 0, 1, 2, 3, \dots$

This system has 4 states (0, 1, 2, 3)


STD of system above:

 

Number of Flip-Flops

 

c: 0, 1, 2, 3, 0, 1, 2, 3, ...

 

How many flip-flops inside box?

- state = output from flops
- 4 states
- output from flops must have at least 4 distinct values
- 2 bits of information = 4 distinct values

→ system requires (at least) 2 flops

Number of flops depends on number of states

Number of Flip-Flops

Number of flops depends on number of states

number of flops = ceiling(\log_2 (#of states))

examples:

3 states system needs at least 2 flops


4 states system needs at least 2 flops

8 states system needs at least 3 flops

5 states system needs at least 3 flops

9-16 states system needs 4 flops


State Transition Diagram

 


$c: 0, 1, 2, 3, 4, 5, 6, 7, 0, 1, 2, \dots$

This system has **8 states** (0, ..., 7)
requires at least **3 flip-flops**

STD of system above:

 

State Transition Diagram

 


c: 0, 1, 2, 3, 2, 1, 0, 1, 2, 3, 2, 1, 0, 1, ...

c output moves up and down in (0, 1, 2, 3)

What are the **states**?


This system has **how many states**?

The states cannot be c anymore

 

when c is 1,
sometimes next c is 0
sometimes next c is 2

State Transition Diagram

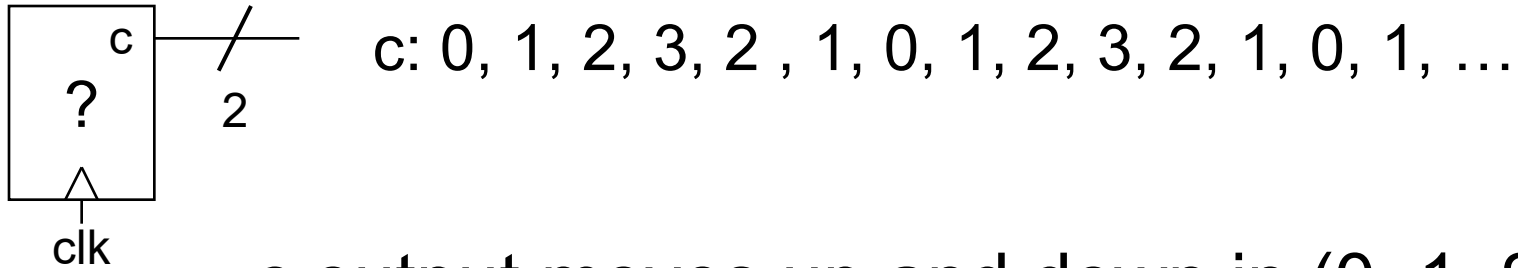

c output moves up and down in (0, 1, 2, 3)


The states must contain BOTH c and DIRECTION
(counting up or down)

State = set of (dynamic) information that is
sufficient for the system to work

Knowing only c (output) is not sufficient


States are NOT the same as outputs

State Transition Diagram

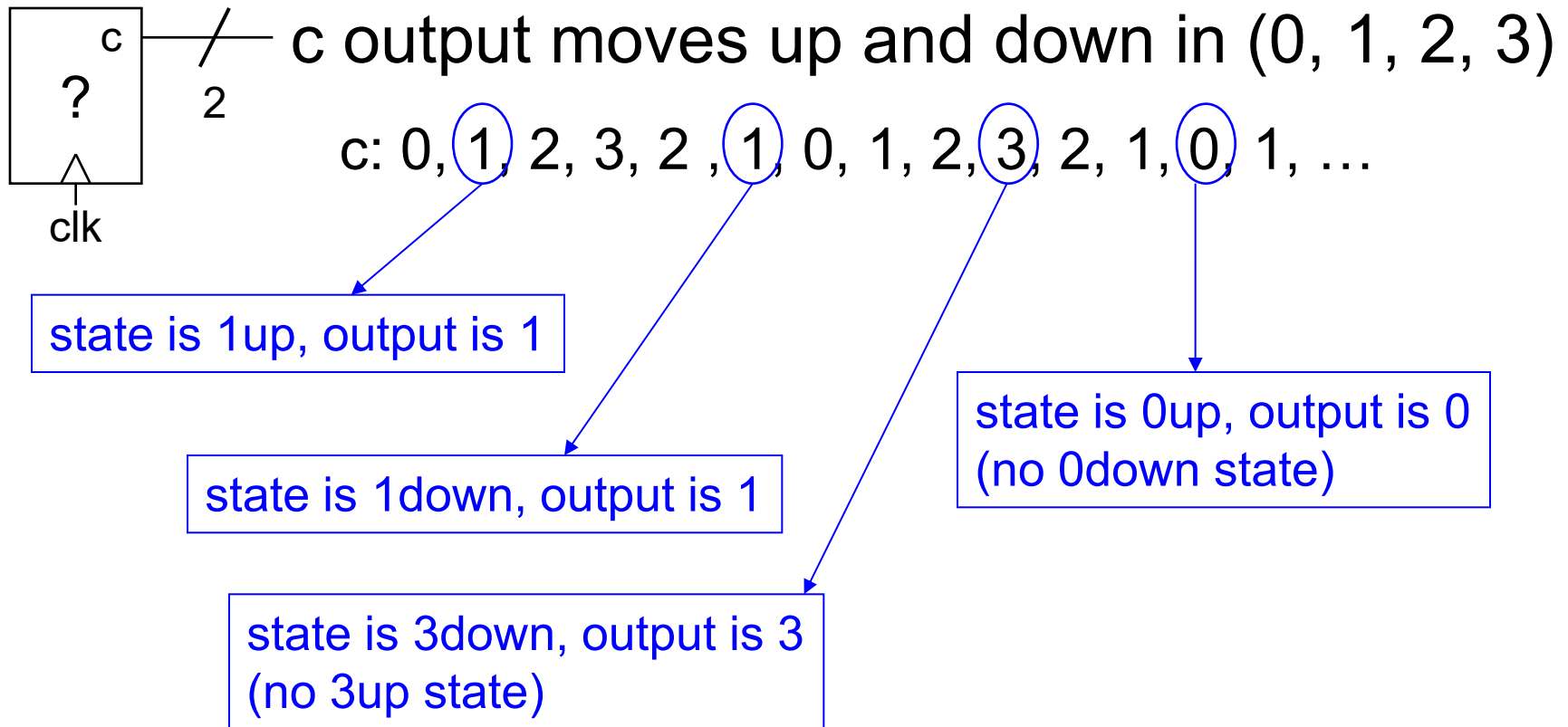


This system needs at least 6 states (3 flops)
0up, 1up, 2up, 3down, 2down, 1down

State Transition Diagram

 

c: 0, 1, 2, 3, 2, 1, 0, 1, 2, 3, 2, 1, 0, 1, ...


Writing STD

 

circles = states

one circle per state


write name and output inside

 

A = 0up, B = 1up, etc.


You can give states any name,
but you **MUST** know what they
mean

State Transition Diagram

 


c: 0, 0, 1, 1, 0, 0, 1, 1, ...

How many states? How many flops?

 

c: $\underbrace{0, 1}_1, \underbrace{0, 0}_2, 1, \underbrace{0, 0, 0}_3, 1, \underbrace{0, 0, 0, 0}_4, 1, \underbrace{0}_1, 1, \dots$


How many states? How many flops?

 



c: $\underbrace{0, 0, \dots, 0}_{999,999}, 1, \underbrace{0, 0, \dots, 0}_{999,999}, 1, \underbrace{0, 0, \dots, 0}_{999,999}, 1$

How many states? How many flops?


Back to Hardware:

 

c: 0, 0, 1, 1, 0, 0, 1, 1, ...

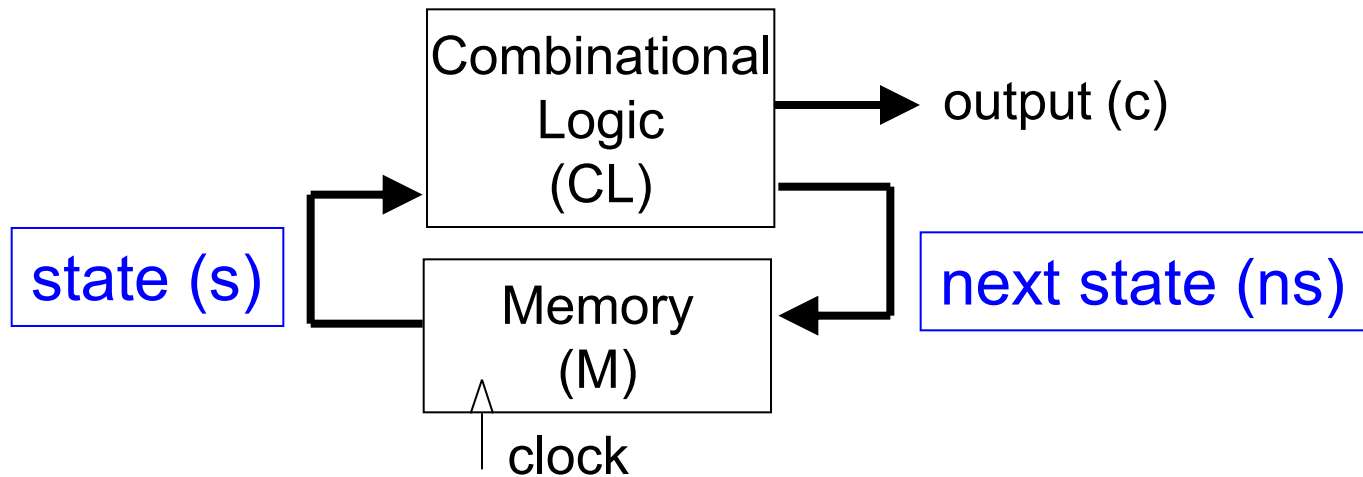 


Back to Hardware:

 

c: 0, 0, 1, 1, 0, 0, 1, 1, ...


2 parts in Combinational Logic

 


Back to Hardware:

2 parts in Combinational Logic


- NSCL (next state CL)
- OCL (output CL)

 

Back to Hardware:

 


Rewrite

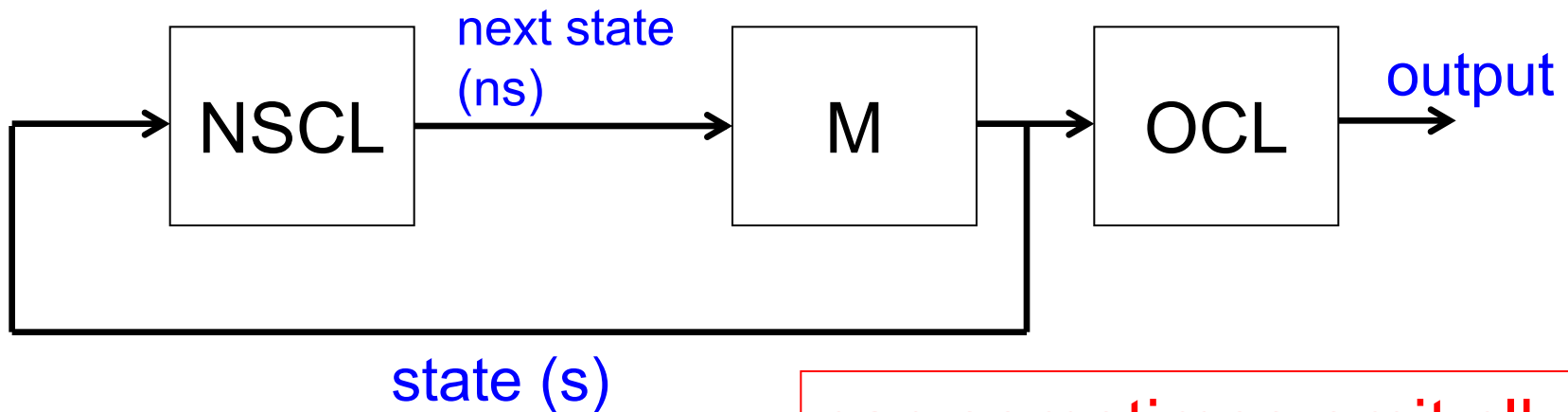

can sometimes omit clk


Back to Hardware:

 


Hardware design:

- Have appropriate # of flops
- Design NSCL $\rightarrow ns = f(s)$
- Design OCL $\rightarrow out = f(s)$

Back to Hardware:

 


Design Example

 


$c: 0, 0, 0, 1, 0, 0, 0, 1, \dots$

- What are the states?
- How many states?
- How many flip-flops?
- Draw the STD

Back to Hardware:

 


Design Example

 



c: 0, 0, 0, 1, ...

STD

 

- 4 states, 2 flip-flops

Back to Hardware:

  

Hardware has 0's & 1's

Hardware does not have A B C D
(state names)


STATE ENCODING is

Mapping states to 0's & 1's

Back to Hardware:

STATE ENCODING is mapping states to 0's & 1's

 
- **minimal encoding** = use as few bits as possible
(4 states, 2 bits will be enough)



- **one hot** = use as many flops as states (4 states, 4 flops)
- other variations on one-hot


Using more flops sometimes make CL design faster
In this course, we will use minimal encoding

Back to Hardware:


 


Minimal State Encoding

A = 00, B = 01, C = 10, D = 11

 

Back to Hardware:

  



A = 00
B = 01
C = 10
D = 11

Back to design

$ns = f(s)$
 $out = f(s)$

Map **ns** as a function of **s**
Map **out** as a function of **s**

Back to Hardware:

  

A = 00
B = 01
C = 10
D = 11




s	ns
A	B
B	C
C	D
D	A




s	ns
00	01
01	10
10	11
11	00

Back to Hardware:

 

State Transition Table

 

A = 00
B = 01
C = 10
D = 11




s	ns
A	B
B	C
C	D
D	A




s	ns
00	01
01	10
10	11
11	00

Remember $ns = f(s)$

Back to Hardware:

 

State Output Table

 

A = 00
B = 01
C = 10
D = 11




s	out
A	0
B	0
C	0
D	1



s	out
00	0
01	0
10	0
11	1

Remember $out = f(s)$

Back to Hardware:

 

State Transition

s	ns
00	01
01	10
10	11
11	00


$$ns = f(s)$$

State Output

s	out
00	0
01	0
10	0
11	1

$$out = f(s)$$

Back to Hardware:

 

State Transition

s	ns
00	01
01	10
10	11
11	00

$$ns = f(s)$$



s_1s_0	ns_1ns_0
00	01
01	10
10	11
11	00

$$ns_1 = f(s_1, s_0)$$
$$ns_0 = f(s_1, s_0)$$


		s_0		
		0	1	
s_1	0	0	1	
	1	1	0	

ns1

		s_0		
		0	1	
s_1	0	1	0	
	1	1	0	

ns0

Back to Hardware:

 

State Transition


		s_0		
		0	1	
s_1	0	0	1	ns1
	1	1	0	

$$\leftarrow ns1 = s0 \wedge s1$$

		s_0		
		0	1	
s_1	0	1	0	ns0
	1	1	0	

$$\leftarrow ns0 = s0'$$

Back to Hardware:

 

State Output

s	out
00	0
01	0
10	0
11	1

$$\text{out} = f(s)$$



s ₁ s ₀	out
00	0
01	0
10	0
11	1

$$\text{out} = f(s_1, s_0)$$




A Karnaugh map for the function $\text{out} = s_1 s_0$. The map is a 2x2 grid with s_1 on the vertical axis and s_0 on the horizontal axis. The top-left cell (0,0) contains 0, the top-right cell (0,1) contains 0, the bottom-left cell (1,0) contains 0, and the bottom-right cell (1,1) contains 1. The label 'out' is in blue at the top right.

$s_1 \backslash s_0$	0	1
0	0	0
1	0	1

$$\text{out} = s_1 s_0$$


Back to Hardware:

 

State Transition


$$ns1 = s0 \wedge s1$$

$$ns0 = s0'$$

 


State Output

$$out = s0 s1$$

 


Back to Hardware:

 

State Transition


$$ns1 = s0 \wedge s1$$

$$ns0 = s0'$$

 

NSCL


Memory

 

M

State Output

$$out = s0 s1$$


 


OCL

Putting it all together:



$$ns1 = s0 \wedge s1 \quad out = s0 s1$$

$$ns0 = s0'$$

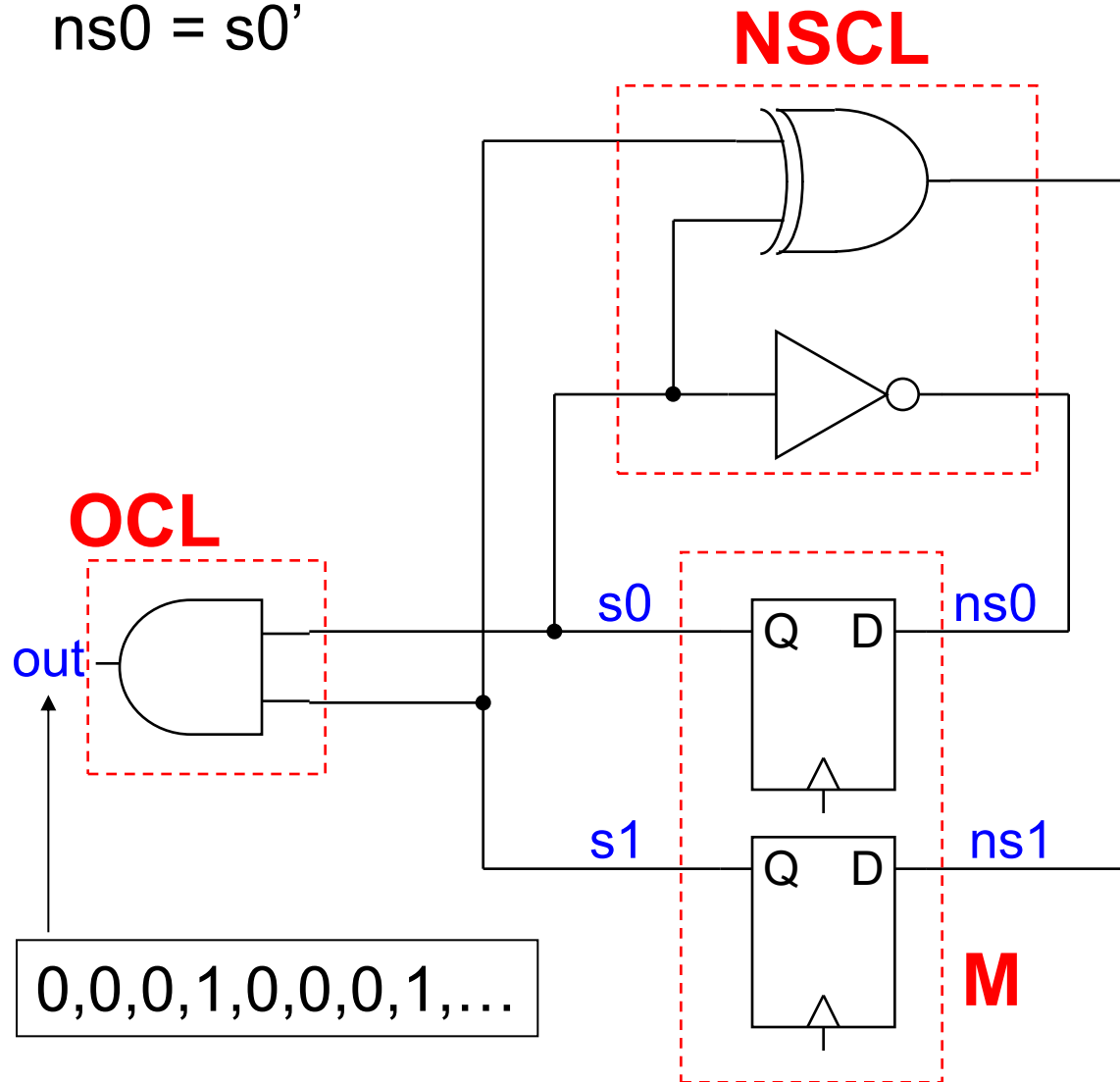 

for synchronous design (all flops running off the same clock), you can omit drawing clock signal



Back to Hardware (Verilog version):

  

A = 00
B = 01
C = 10
D = 11

```
module fsm(clk, out);  
    input clk;  
    output [1:0] out;  
  
    //  
    // NSCL, M, and OCL design  
    //  
  
endmodule
```


Back to Hardware (Verilog version):

  



A = 00
B = 01
C = 10
D = 11

```
reg [1:0] s, ns;
```

```
always @(posedge clk)  
    s <= #1 ns;
```

M design

Back to Hardware (Verilog version):

 
 


A = 00
B = 01
C = 10
D = 11

```
reg out;  
  
always @ (s)  
    if (s == 2'b11)  
        out = 1;  
    else  
        out = 0;
```

OCL design

Back to Hardware (Verilog version):

 
 


A = 00
B = 01
C = 10
D = 11

```
always @ (s)
  case (s)
    2'b00: ns = 2'b01;
    2'b01: ns = 2'b10;
    2'b10: ns = 2'b11;
    2'b11: ns = 2'b00;
  endcase
```

NSCL design

Back to Hardware (Verilog version):

  

A = 00
B = 01
C = 10
D = 11

```
module fsm(clk, out);
    input clk;
    output [1:0] out;
    reg [1:0] s, ns;
    reg out;

    // M (Memory)
    always @(posedge clk)
        s <= #1 ns;

    // OCL (Output CL)
    always @(s)
        if (s == 2'b11)
            out = 1;
        else
            out = 0;
endmodule
```

```
// NSCL (Next State CL)
always @(s)
    case (s)
        2'b00: ns = 2'b01;
        2'b01: ns = 2'b10;
        2'b10: ns = 2'b11;
        2'b11: ns = 2'b00;
    endcase
endmodule
```