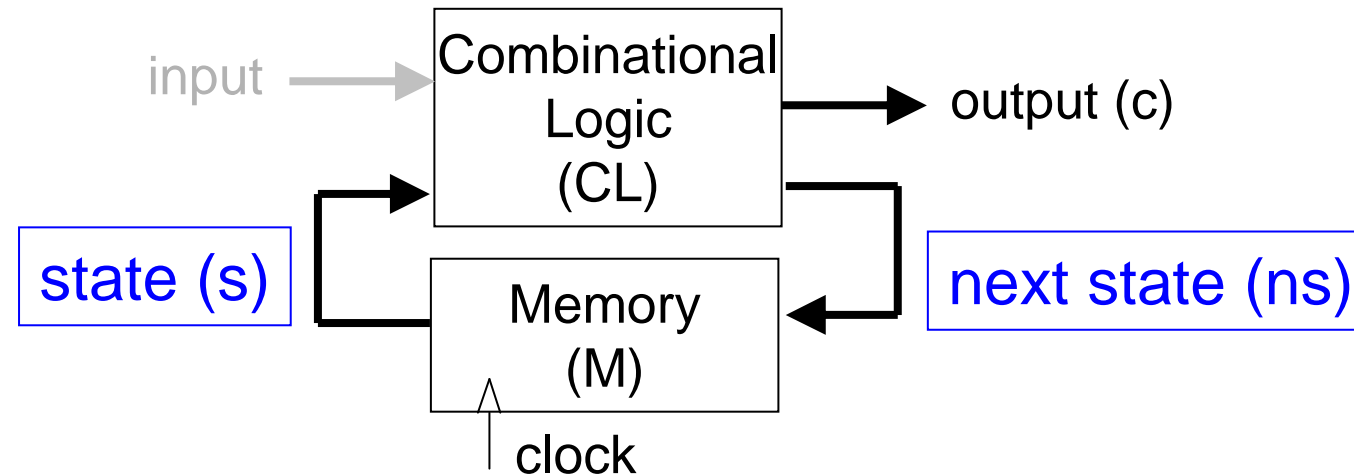


## 10 Finite State Machine (FSM) II


- Inputs & Changes to NSCL and OCL
- Inputs & Changes to STD
  - Example: Stop/Go counter
- Output Models: Moore/Mealy/Mixed
- Unused States and Reset
  - Examples: Vending Machine
  - Sequence Recognizer
- Next State as Outputs
- Shift Registers and SERDES

Previously on lecture set 09:

## FSM with no input



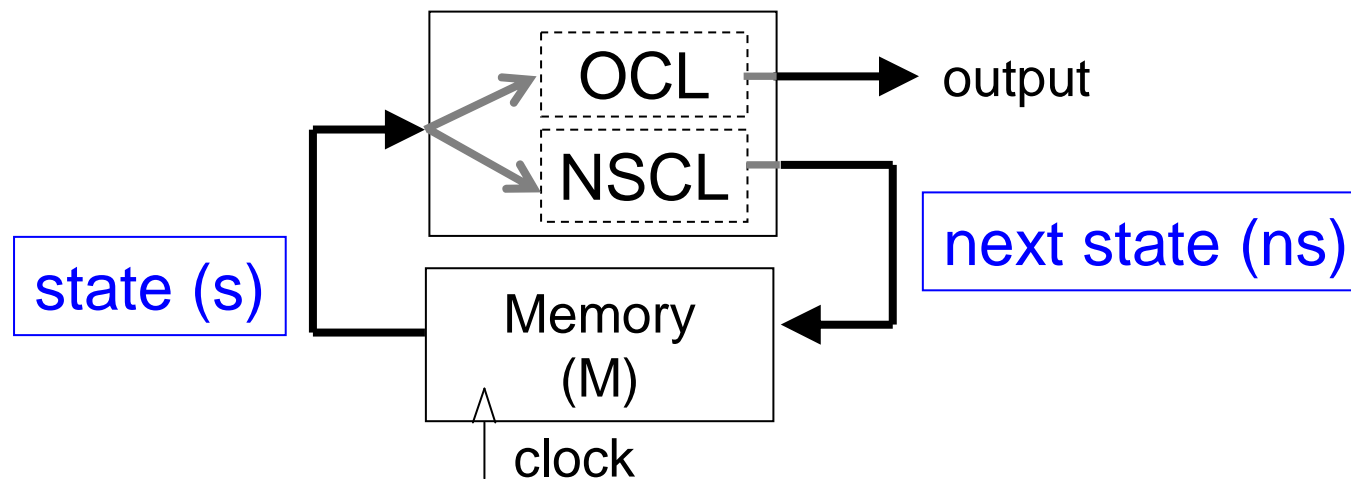
## FSM with no input separated into NSCL & OCL



## FSM with input example:

Example: - stop/go 0, 1, 2, 3 counter

 


When run = 1, c = 0, 1, 2, 3, 0, 1, 2, 3, ...  
When run = 0, c holds the previous value

clk#	1	2	3	4	5	6	7	8	9	1	1	1	1	1	1	1	1
run	1	1	1	1	1	1	1	0	0	0	0	1	0	1	1	1	0
c	0	1	2	3	0	1	2	3	3	3	3	3	0	0	1	2	3

**input controls behavior of FSM**

## FSM with input example:

Example: - stop/go 0, 1, 2, 3 counter

 

When  $\text{run} = 1$ ,  $c = 0, 1, 2, 3, 0, 1, 2, 3, \dots$


When  $\text{run} = 0$ ,  $c$  holds the previous value

State = ?

How many states?

How many flops?

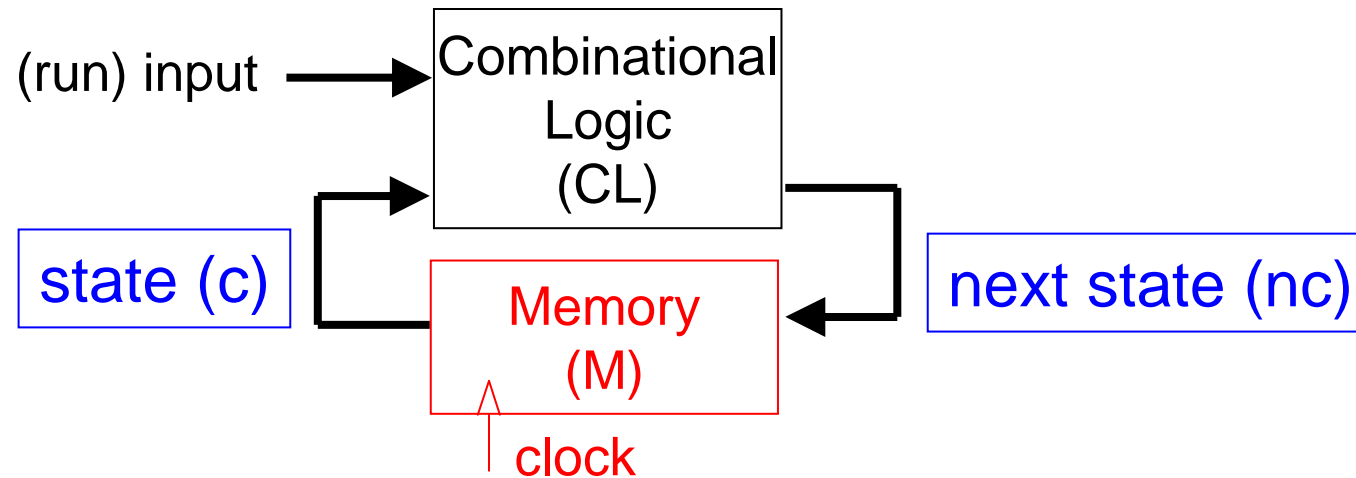FSM example: stop/go counter  $c: 0, 1, 2, 3, \dots$




What does Mike do?

store  $nc$  that CLaire gives in this clock cycle, and give it back to CLaire next clock cycle, calling it  $c$

 **Mike works in the same way as before**

FSM example: stop/go counter c: 0, 1, 2, 3, ...




What does CLaire do?

Look at **c** AND **run** (input) and figure out what **nc** should be

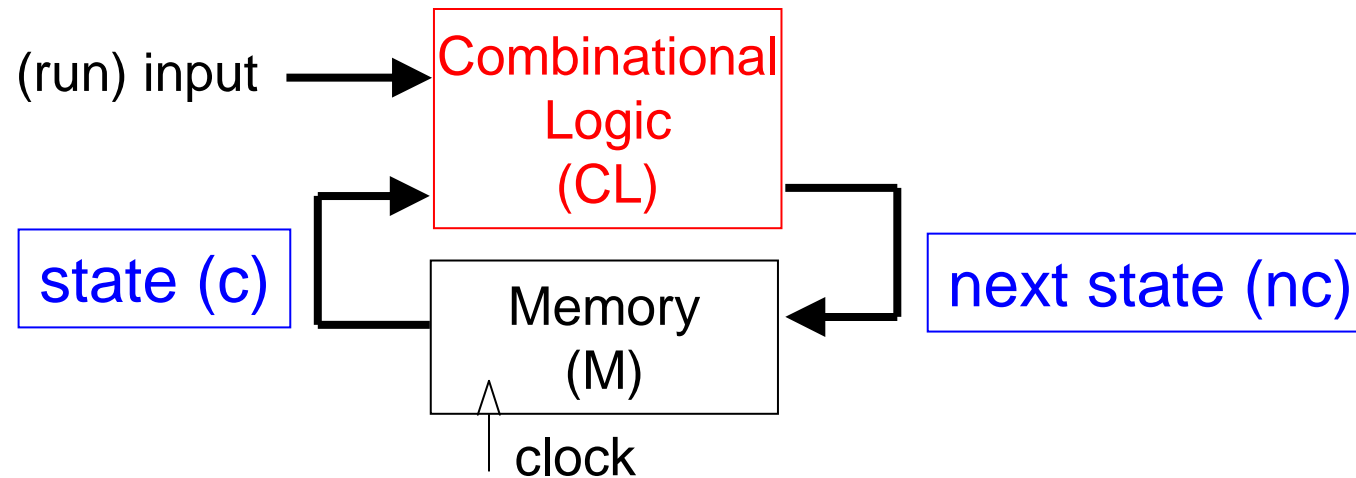
**CLaire needs to look at to look at both input and state to determine next state**

FSM example: stop/go counter  $c$ : 0, 1, 2, 3, ...




---

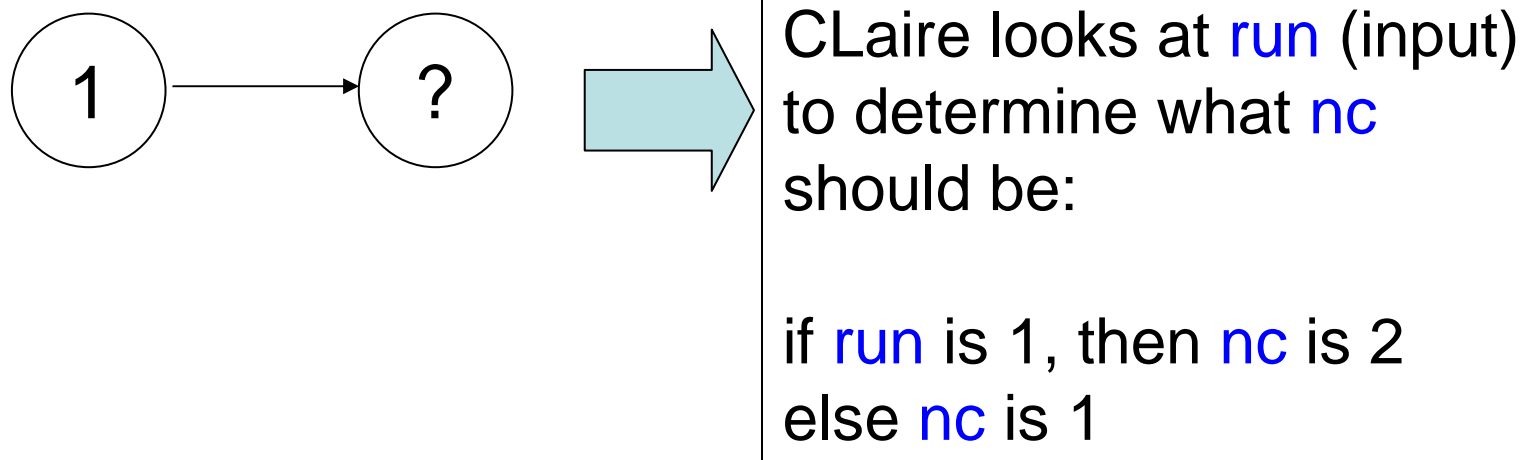CLaire sees  $c=1$ , CLaire needs to write  $nc$




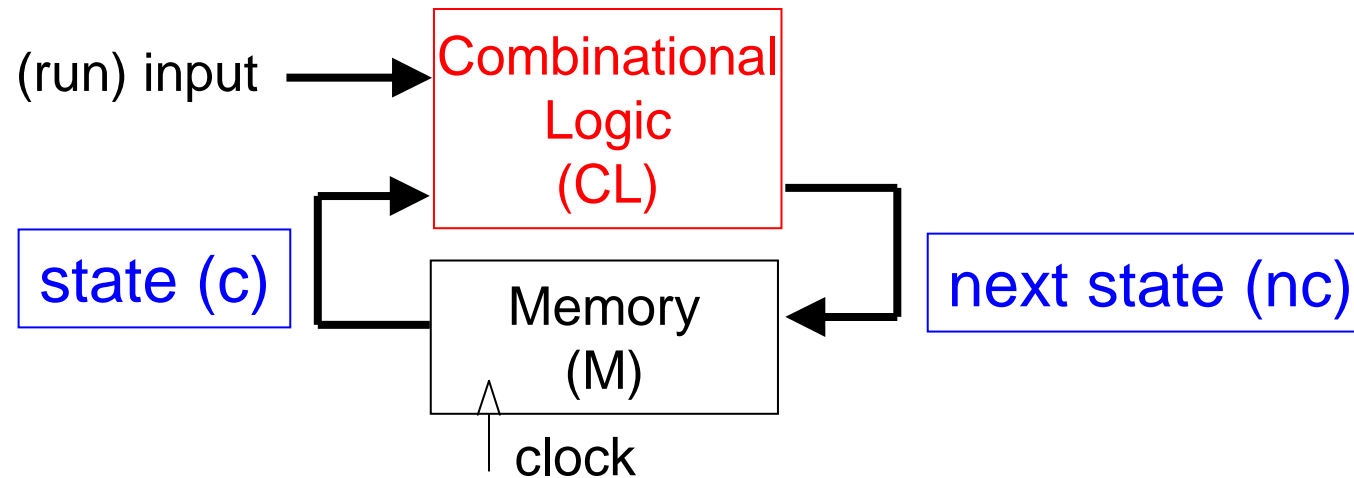FSM example: stop/go counter  $c: 0, 1, 2, 3, \dots$



---

 CLaire sees  $c=1$ , CLaire needs to write  $nc$




**Input creates more arcs**

1-bit input = 2 possibilities  
= 2 arcs coming out of each state

**$n$ -bit input  $\rightarrow 2^n$  arcs out from each state**



## FSM example:

 


If the system has 1-bit input, then every state must have 2 arcs coming out.  
Arcs going in do not matter.

For system with  $n$ -bit input, every state must have  $2^n$  arcs coming out.


## FSM with inputs example:

Example: - stop/go 0, 1, 2, 3 counter

 



When run = 1, c = 0, 1, 2, 3, 0, 1, 2, 3, ...  
When run = 0, c holds the previous value

STD of stop/go  
counter

 

## FSM with inputs example:

Example: - stop/go 0, 1, 2, 3 counter

 
 


## let us simulate

[illegible]

## FSM with inputs example:

Example: - stop/go 0, 1, 2, 3 counter

 
 


## let us simulate

clk#	1	2	3	4	5	6	7	8	9	1	1	1	1	1	1	1	1	1
run	1	1	1	1	1	1	1	0	0	0	0	1	0	1	1	1	0	0
c	0	?																

## FSM with inputs example:

Example: - stop/go 0, 1, 2, 3 counter

 
 


let us simulate

clk#	1	2	3	4	5	6	7	8	9	1	1	1	1	1	1	1	1	1
run	1	1	1	1	1	1	1	0	0	0	0	1	0	1	1	1	0	0
c	0	1																

## FSM with inputs example:

Example: - stop/go 0, 1, 2, 3 counter

 
 


## let us simulate

[illegible]

## FSM with inputs example:

Example: - stop/go 0, 1, 2, 3 counter

 
 


## let us simulate

[illegible][illegible]

## FSM with inputs example:

Example: - stop/go 0, 1, 2, 3 counter

  



## let us simulate

[illegible]



## FSM with inputs example:

Example: - stop/go 0, 1, 2, 3 counter

 
 


let us simulate

clk#	1	2	3	4	5	6	7	8	9	1	1	1	1	1	1	1	1
run	1	1	1	1	1	1	1	0	0	0	0	1	0	1	1	1	0
c	0	1	2	3	0	1	2	3	3	3							

## FSM with inputs example:

Example: - stop/go 0, 1, 2, 3 counter

 
 


let us simulate

clk#	1	2	3	4	5	6	7	8	9	1	1	1	1	1	1	1	1
run	1	1	1	1	1	1	1	0	0	0	0	1	0	1	1	1	0
c	0	1	2	3	0	1	2	3	3	3	3						

## FSM with inputs example:

Example: - stop/go 0, 1, 2, 3 counter

 
 


let us simulate

clk#	1	2	3	4	5	6	7	8	9	1	1	1	1	1	1	1	1
run	1	1	1	1	1	1	1	0	0	0	0	1	0	1	1	1	0
c	0	1	2	3	0	1	2	3	3	3	3	3	0	0	1	2	3

## FSM with inputs example:

Example: - stop/go 0, 1, 2, 3 counter

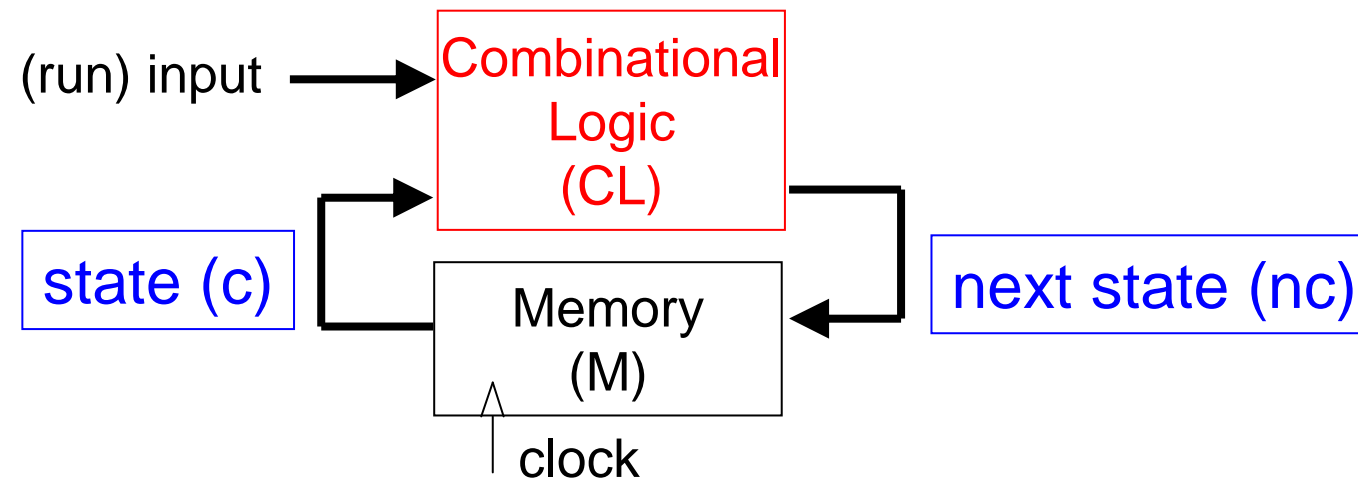 


**NSCL: next\_state = f(input, state)**

## FSM with inputs (summary):

- inputs mean more arcs
- n-bit input  $\rightarrow 2^n$  arcs out from each state
- no (0) input  $\rightarrow 1$  arc out from each state
- NSCL is


$$ns = f(in, s)$$

## Output Models:

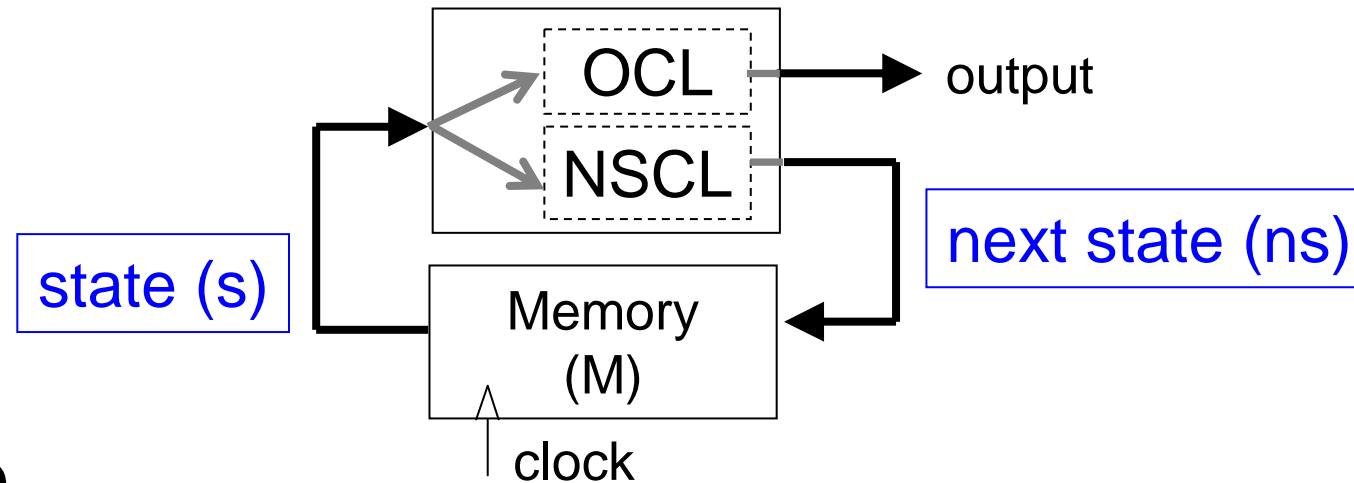


Rewrite

---

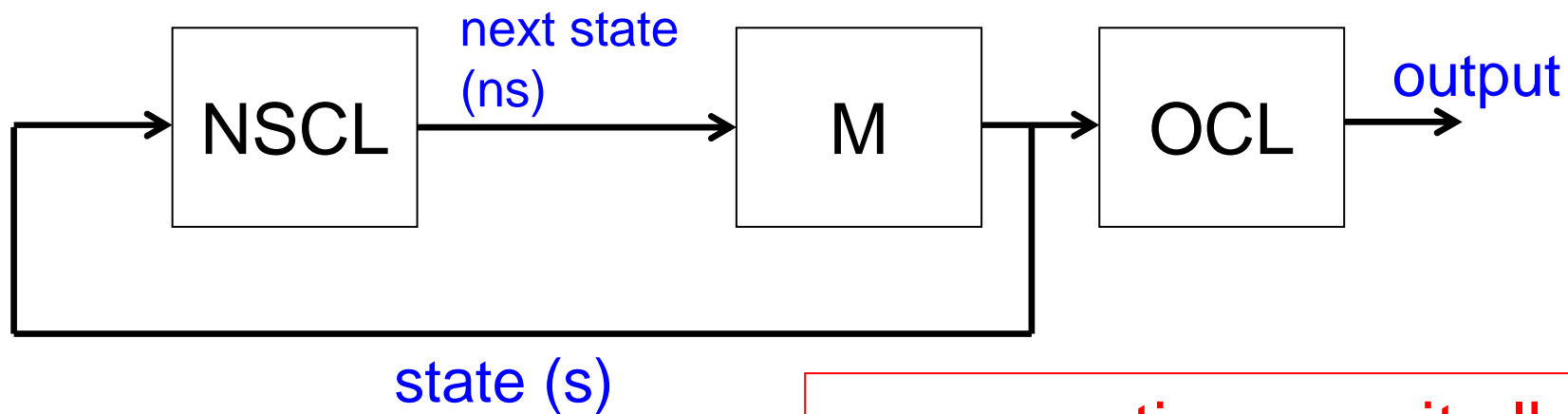


can sometimes omit clk

## Output Models:

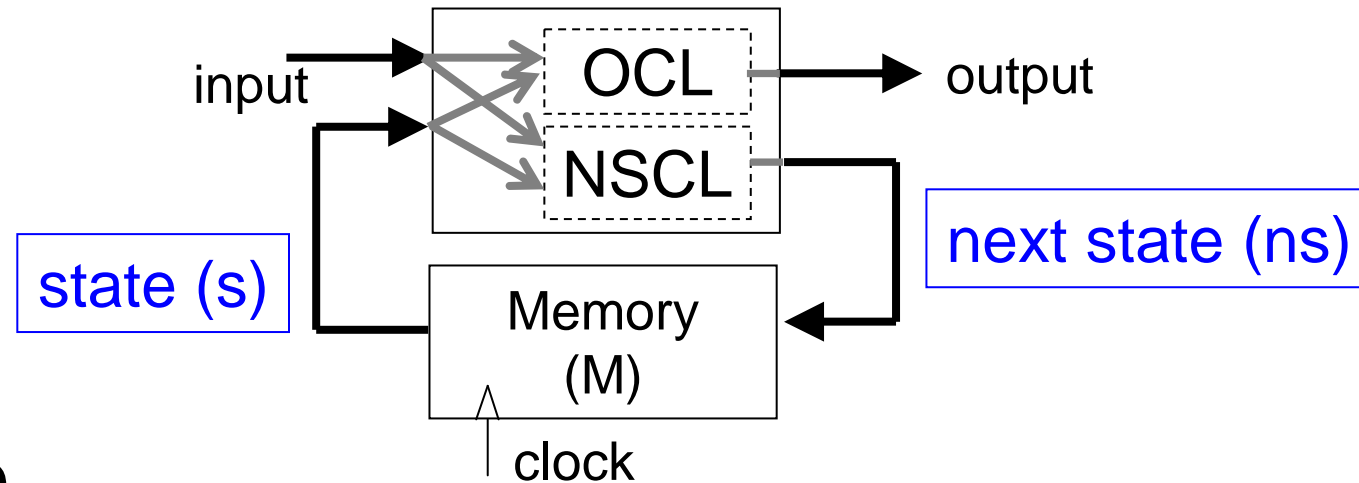


Rewrite

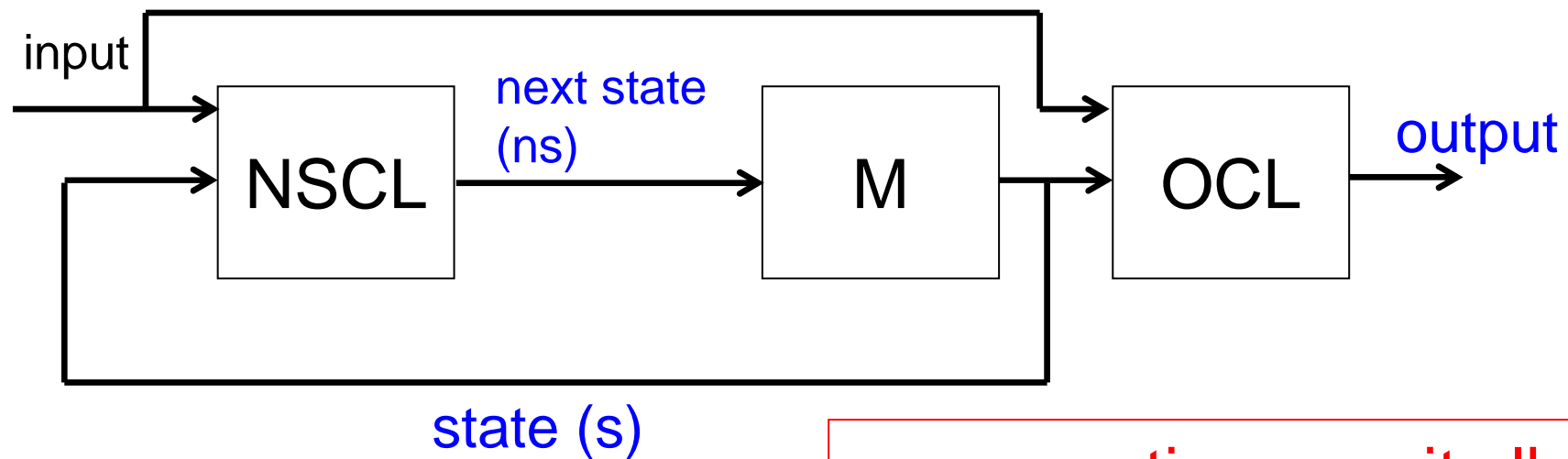


can sometimes omit clk

## Output Models:

 

**MEALY OUTPUT MODEL:  $out = f(in, s)$**

---

 


**MOORE OUTPUT MODEL:  $out = f(s)$**


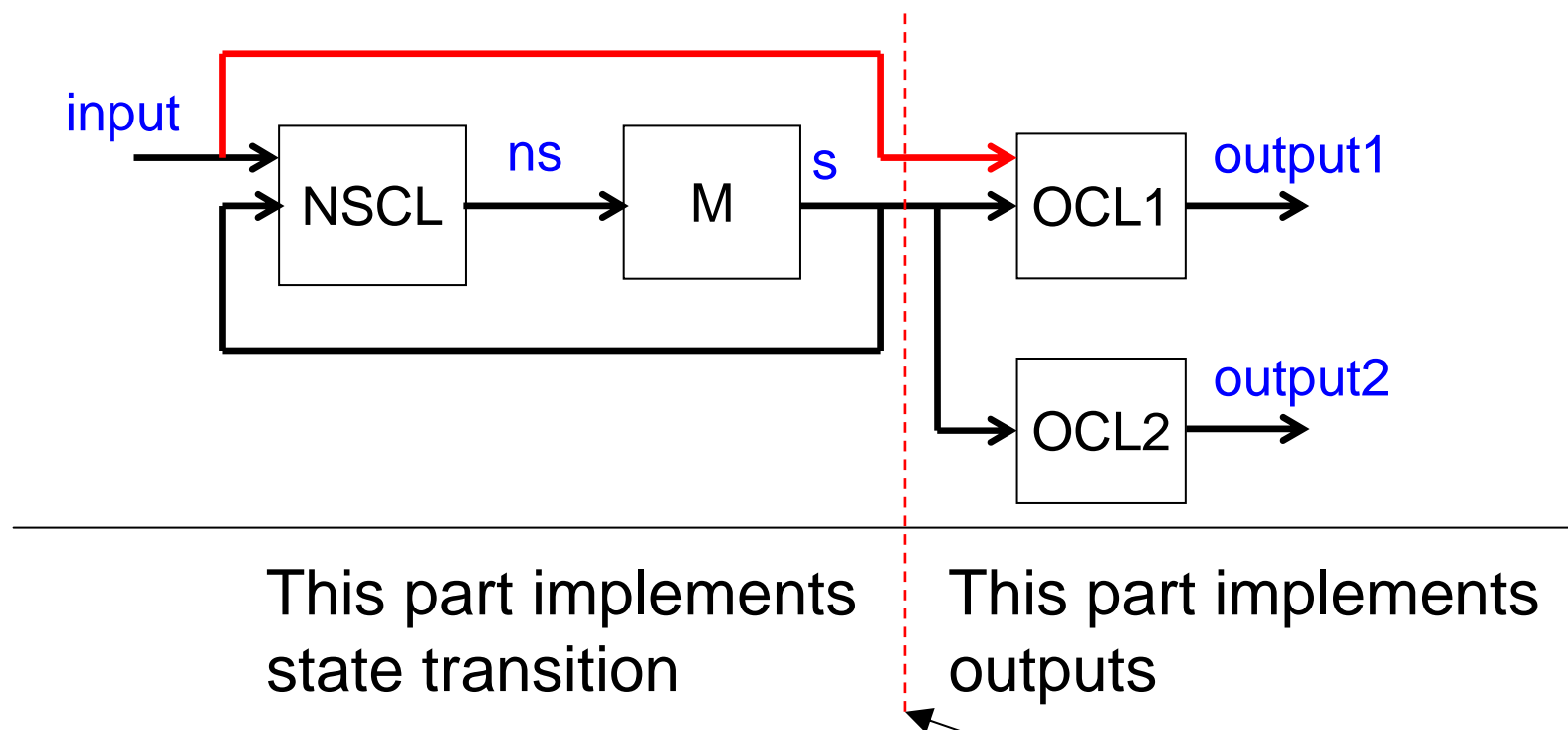
# Output Models:


Mixing many output types is possible.

FSM does not need to be all Moore or all Mealy.



**Once information passes through dotted line, it does not come back.**

## Outputs on STDs:

 


**MOORE OUTPUT MODEL:  $\text{out} = f(s)$**


---

- know the state, know the output
- so output is written together with state
- output will lag input by at least 1 clock cycle

Moore output  
written here

 


## Outputs on STDs:

 

 
**MEALY OUTPUT MODEL:  $out = f(in, s)$**

- must know both state and input to know output
- so output is written together with arc
- output can respond to input within same clock cycle



# Mealy FSM example:

 Example: - **Mealy** stop/go 0, 1, 2, 3 counter




When run = 1, c = 0, 1, 2, 3, 0, 1, 2, 3, ...  
When run = 0, c holds the previous value

clk#	1	2	3	4	5	6	7	8	9	1	1	1	1	1	1	1	1
run	1	1	1	1	1	1	1	0	0	0	0	1	0	1	1	1	0
c	0	1	2	3	0	1	2	2	2	2	2	3	3	0	1	2	2

## Mealy FSM example:

 
Example: - **Mealy** stop/go 0, 1, 2, 3 counter:

- States are no longer the outputs
- Can stop and start immediately (Mealy output)



## Mealy FSM example:

 Example: - **Mealy** stop/go 0, 1, 2, 3 counter:




let us simulate

clk#	1	2	3	4	5	6	7	8	9	1	1	1	1	1	1	1	1	1
										0	1	2	3	4	5	6	7	8
run	1	1	1	1	1	1	1	0	0	0	0	1	0	1	1	1	0	0
state	A																	
output																		

## Mealy FSM example:

 
Example: - **Mealy** stop/go 0, 1, 2, 3 counter:



clk#	1	2	3	4	5	6	7	8	9	1	1	1	1	1	1	1	1	1
run	1	1	1	1	1	1	1	0	0	0	0	1	0	1	1	1	0	0
state	A																	
output	?																	

## Mealy FSM example:

 Example: - **Mealy** stop/go 0, 1, 2, 3 counter:




clk#	1	2	3	4	5	6	7	8	9	1	1	1	1	1	1	1	1	1
										0	1	2	3	4	5	6	7	8
run	1	1	1	1	1	1	1	0	0	0	0	1	0	1	1	1	0	0
state	A																	
output	0																	



## Mealy FSM example:

 
Example: - **Mealy** stop/go 0, 1, 2, 3 counter:



clk#	1	2	3	4	5	6	7	8	9	1	1	1	1	1	1	1	1	1
										0	1	2	3	4	5	6	7	8
run	1	1	1	1	1	1	1	0	0	0	0	1	0	1	1	1	0	0
state	A	B																
output	0																	

## Mealy FSM example:

 
Example: - **Mealy** stop/go 0, 1, 2, 3 counter:



clk#	1	2	3	4	5	6	7	8	9	1	1	1	1	1	1	1	1	1
										0	1	2	3	4	5	6	7	8
run	1	1	1	1	1	1	1	0	0	0	0	1	0	1	1	1	0	0
state	A	B																
output	0	1																


## Mealy FSM example:

Example: - **Mealy** stop/go 0, 1, 2, 3 counter:

 [illegible]

## Mealy FSM example:

 Example: - **Mealy** stop/go 0, 1, 2, 3 counter:




observation:  
need only input & state for next state  
let's finish up state first

[illegible]


## Mealy FSM example:

Example: - **Mealy** stop/go 0, 1, 2, 3 counter:

 [illegible]

## Mealy FSM example:

 
Example: - **Mealy** stop/go 0, 1, 2, 3 counter:



clk#	1	2	3	4	5	6	7	8	9	1	1	1	1	1	1	1	1	1
										0	1	2	3	4	5	6	7	8
run	1	1	1	1	1	1	1	0	0	0	0	1	0	1	1	1	0	0
state	A	B	C	D	A													
output	0	1	2															


## Mealy FSM example:

Example: - **Mealy** stop/go 0, 1, 2, 3 counter:

 [illegible]

## Mealy FSM example:


Example: - **Mealy** stop/go 0, 1, 2, 3 counter:

 [illegible]




## Mealy FSM example:

Example: - **Mealy** stop/go 0, 1, 2, 3 counter:

 [illegible]


## Mealy FSM example:

Example: - **Mealy** stop/go 0, 1, 2, 3 counter:

 [illegible]


## Mealy FSM example:

Example: - **Mealy** stop/go 0, 1, 2, 3 counter:

 [illegible]


## Mealy FSM example:

Example: - **Mealy** stop/go 0, 1, 2, 3 counter:

 [illegible]


## Mealy FSM example:

Example: - **Mealy** stop/go 0, 1, 2, 3 counter:

 [illegible]


## Mealy FSM example:

Example: - **Mealy** stop/go 0, 1, 2, 3 counter:

 [illegible]


## Mealy FSM example:

Example: - **Mealy** stop/go 0, 1, 2, 3 counter:

 [illegible]

## Mealy FSM example:


Example: - **Mealy** stop/go 0, 1, 2, 3 counter:

 [illegible]




## Mealy FSM example:

Example: - **Mealy** stop/go 0, 1, 2, 3 counter:

 [illegible]


## Mealy FSM example:

Example: - **Mealy** stop/go 0, 1, 2, 3 counter:

 [illegible]


## Mealy FSM example:

Example: - **Mealy** stop/go 0, 1, 2, 3 counter:

 [illegible]

## Mealy FSM example:

 Example: - **Mealy** stop/go 0, 1, 2, 3 counter:




we need to know  
input and state to know output

[illegible]

## Mealy FSM example:

 
Example: - **Mealy** stop/go 0, 1, 2, 3 counter:



clk#	1	2	3	4	5	6	7	8	9	1	1	1	1	1	1	1	1	1
run	1	1	1	1	1	1	1	0	0	0	0	1	0	1	1	1	0	0
state	A	B	C	D	A	B	C	D	D	D	D	D	A	A	B	C	D	D
output	0	1	2	3														


## Mealy FSM example:

Example: - **Mealy** stop/go 0, 1, 2, 3 counter:

 [illegible]


## Mealy FSM example:

Example: - **Mealy** stop/go 0, 1, 2, 3 counter:

 [illegible]

## Mealy FSM example:

Example: - **Mealy** stop/go 0, 1, 2, 3 counter:

 
[illegible]





## Mealy FSM example:

 
Example: - **Mealy** stop/go 0, 1, 2, 3 counter:



clk#	1	2	3	4	5	6	7	8	9	1	1	1	1	1	1	1	1	1
										0	1	2	3	4	5	6	7	8
run	1	1	1	1	1	1	1	0	0	0	0	1	0	1	1	1	0	0
state	A	B	C	D	A	B	C	D	D	D	D	D	A	A	B	C	D	D
output	0	1	2	3	0	1	2	2	2	2	2							

## Mealy FSM example:

 
Example: - **Mealy** stop/go 0, 1, 2, 3 counter:



clk#	1	2	3	4	5	6	7	8	9	1	1	1	1	1	1	1	1	1
										0	1	2	3	4	5	6	7	8
run	1	1	1	1	1	1	1	0	0	0	0	1	0	1	1	1	0	0
state	A	B	C	D	A	B	C	D	D	D	D	D	A	A	B	C	D	D
output	0	1	2	3	0	1	2	2	2	2	2	3						

## Mealy FSM example:

 
Example: - **Mealy** stop/go 0, 1, 2, 3 counter:



clk#	1	2	3	4	5	6	7	8	9	1	1	1	1	1	1	1	1	1
										0	1	2	3	4	5	6	7	8
run	1	1	1	1	1	1	1	0	0	0	0	1	0	1	1	1	0	0
state	A	B	C	D	A	B	C	D	D	D	D	D	A	A	B	C	D	D
output	0	1	2	3	0	1	2	2	2	2	2	3	3					

## Mealy FSM example:

 
Example: - **Mealy** stop/go 0, 1, 2, 3 counter:



clk#	1	2	3	4	5	6	7	8	9	1	1	1	1	1	1	1	1	1
										0	1	2	3	4	5	6	7	8
run	1	1	1	1	1	1	1	0	0	0	0	1	0	1	1	1	0	0
state	A	B	C	D	A	B	C	D	D	D	D	D	A	A	B	C	D	D
output	0	1	2	3	0	1	2	2	2	2	2	3	3	0				

## Mealy FSM example:

 
Example: - **Mealy** stop/go 0, 1, 2, 3 counter:



clk#	1	2	3	4	5	6	7	8	9	1	1	1	1	1	1	1	1	1
										0	1	2	3	4	5	6	7	8
run	1	1	1	1	1	1	1	0	0	0	0	1	0	1	1	1	0	0
state	A	B	C	D	A	B	C	D	D	D	D	D	A	A	B	C	D	D
output	0	1	2	3	0	1	2	2	2	2	2	3	3	0	1			

## Mealy FSM example:

 
Example: - **Mealy** stop/go 0, 1, 2, 3 counter:



clk#	1	2	3	4	5	6	7	8	9	1	1	1	1	1	1	1	1	1
										0	1	2	3	4	5	6	7	8
run	1	1	1	1	1	1	1	0	0	0	0	1	0	1	1	1	0	0
state	A	B	C	D	A	B	C	D	D	D	D	D	A	A	B	C	D	D
output	0	1	2	3	0	1	2	2	2	2	2	3	3	0	1	2		

## Mealy FSM example:

 Example: - **Mealy** stop/go 0, 1, 2, 3 counter:




clk#	1	2	3	4	5	6	7	8	9	1	1	1	1	1	1	1	1	1
										0	1	2	3	4	5	6	7	8
run	1	1	1	1	1	1	1	0	0	0	0	1	0	1	1	1	0	0
state	A	B	C	D	A	B	C	D	D	D	D	D	A	A	B	C	D	D
output	0	1	2	3	0	1	2	2	2	2	2	3	3	0	1	2	2	



## Mealy FSM example:

 Example: - **Mealy** stop/go 0, 1, 2, 3 counter:




clk#	1	2	3	4	5	6	7	8	9	1	1	1	1	1	1	1	1	1
										0	1	2	3	4	5	6	7	8
run	1	1	1	1	1	1	1	0	0	0	0	1	0	1	1	1	0	0
state	A	B	C	D	A	B	C	D	D	D	D	D	A	A	B	C	D	D
output	0	1	2	3	0	1	2	2	2	2	2	3	3	0	1	2	2	2

# Mealy FSM example:

 Example: - **Mealy** stop/go 0, 1, 2, 3 counter:

It's possible to have different outputs with different inputs, even when the machine is in the same state




clk#	1	2	3	4	5	6	7	8	9	1	1	1	1	1	1	1	1	1
										0	1	2	3	4	5	6	7	8
run	1	1	1	1	1	1	1	0	0	0	0	1	0	1	1	1	0	0
state	A	B	C	D	A	B	C	D	D	D	D	D	A	A	B	C	D	D
output	0	1	2	3	0	1	2	2	2	2	2	3	3	0	1	2	2	2

# Mealy and Moore Comparison:


## Mealy

clk#	1	2	3	4	5	6	7	8	9	1	1	1	1	1	1	1	1
run	1	1	1	1	1	1	1	0	0	0	0	1	0	1	1	1	0
state	A	B	C	D	A	B	C	D	D	D	D	D	A	A	B	C	D
output	0	1	2	3	0	1	2	2	2	2	2	3	3	0	1	2	2

 

## Moore

clk#	1	2	3	4	5	6	7	8	9	1	1	1	1	1	1	1	1
run	1	1	1	1	1	1	1	0	0	0	0	1	0	1	1	1	0
c	0	1	2	3	0	1	2	3	3	3	3	3	0	0	1	2	3

 

## Mealy and Moore Comparison:

clk#	1	2	3	4	5	6	7	8	9	1	1	1	1	1	1	1	1
run	1	1	1	1	1	1	1	0	0	0	0	1	0	1	1	1	0
Moore out	0	1	2	3	0	1	2	3	3	3	3	3	0	0	1	2	3
Mealy out	0	1	2	3	0	1	2	2	2	2	2	3	3	0	1	2	2


## Mealy and Moore Comparison:

clk#	1	2	3	4	5	6	7	8	9	1	1	1	1	1	1	1	1
run	1	1	1	1	1	1	1	0	0	0	0	1	0	1	1	1	0
Moore out	0	1	2	3	0	1	2	3	3	3	3	3	0	0	1	2	3
Mealy out	0	1	2	3	0	1	2	2	2	2	2	3	3	0	1	2	2

### Observations:


- When the 2 machines are running (run = 1), outputs are the same
- Moore machine stops and starts with one clock delay, but Mealy machine has no delay.

## Unused states and reset:

 


What are the states? How many flops?

## Unused states and reset:

 


What are the states? How many flops? **3 flops**

STD is

 


**but, 3 flops = 8 states**

## Unused states and reset:

 


What are the states? How many flops? **3 flops**

STD is

 




## Unused states and reset:

 


What are the states? How many flops? **3 flops**

STD is

 


## Unused states and reset:

 


What are the states? How many flops? **3 flops**

STD is

 


One possible example


## Unused states and reset:

 

 
When the circuit is powered on, the initial state is unknown. Why?




## Unused states and reset:

 

 
When the circuit is powered on, the initial state is unknown. Why? **flip flop outputs = state**




## Unused states and reset:

 

 
When the circuit is powered on, the initial state is unknown. Why? **flip flop outputs = state**




## Unused states and reset:

 

 
When the circuit is powered on, the initial state is unknown. Why? **flip flop outputs = state**



## Unused states and reset:

 


 When the circuit is powered on, the initial state is unknown. Why? **flip flop outputs = state**




**NOT WHAT WE WANT!!!**

## Unused states and reset:

 


 Even worse, the same circuits starting up at the same time may act differently! → No longer singing the same song






## Unused states and reset:

 


 Most of the time, we want to be able to control the start up behavior: start from this state at this time...



 
## Unused states and reset:

- We modify flip flops (their outputs = state), to start up at a designated place, given a reset signal.
- reset is an external signal into FSM (to the flops only) to force FSM to go to a particular state
- reset is modeled as an arc. like this:  $R \longrightarrow$



 
## Unused states and reset:

- Now flip-flops needs reset in addition to clock
- reset is not considered an “input” to FSM (neither is clock)




 After reset, FSM is guaranteed  
so start in its initial state  
also called reset state


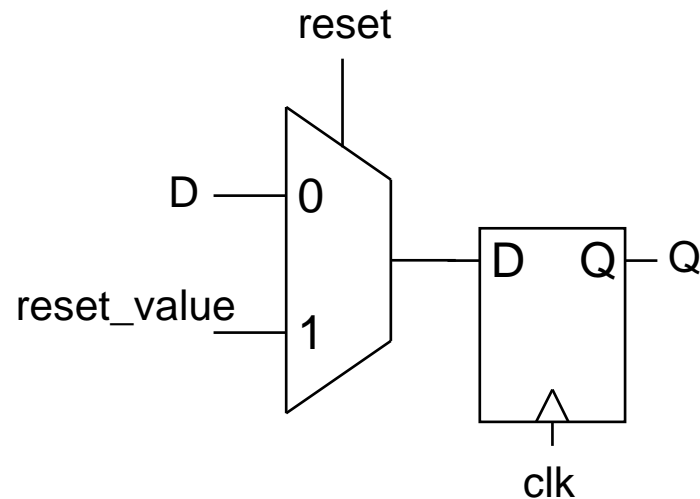
## Unused states and reset:

- some flip-flops need reset in addition to clock
- reset is not considered an “input” to FSM (neither is clock)
- flip-flop with reset is designed as follow:



```
always @(posedge clk)
    if (reset)
        q <= #1 reset_value;
    else
        q <= #1 d;
```

Think about this as a flip-flop with reset, not a MUX and a flop

## Unused states and reset:

- if the reset value is never changed, we can simplify

